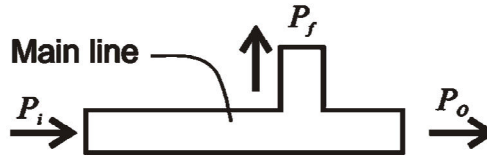


Directional Couplers

Forward



Coupling $C = 10 \log_{10} \frac{P_f}{P_i}$ Typical values: 3, 6, 10, 20, 50 dB

Backward




Directivity $D = 10 \log_{10} \frac{P_f}{P_b}$ Typical values: 50 dB and higher

Talking Points

- Passive
- Frequency dependence
- Insertion loss
- Isolation
- Measurement, tap off signal for STALO

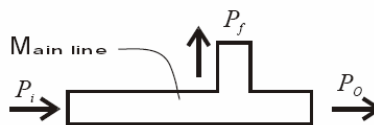Question. The coupling C of the directional coupler below is 40 dB, and the incident power is 10 kW. What is the power at the forward (coupled port) and what is the power at the mainline port?



Solution. A coupling $C = 40$ dB is equal to a ratio of 10^4 . Even though the sign is positive, it is implied that this ratio is an attenuation. This was pointed out in class. Thus, of the $10 \text{ kW} = 10^4 \text{ W}$ flowing into the coupler, $10^4/10^4 = 1 \text{ W}$ flows out P_f . The rest ($10^4 - 1 = 9,999 \text{ W}$) flows out P_o . (4 points total)

